 


Chapter 2


Sequential Circuits and Flip-flops

The R-S flip-flop




S	R	Q	Q'
1	0	1	0
0	0	1	0 (after SR= 10)
0	1	0	1
0	0	0	1(after SR=01)
1	1	0	0 (Disallowed)

The R-S flip-flop

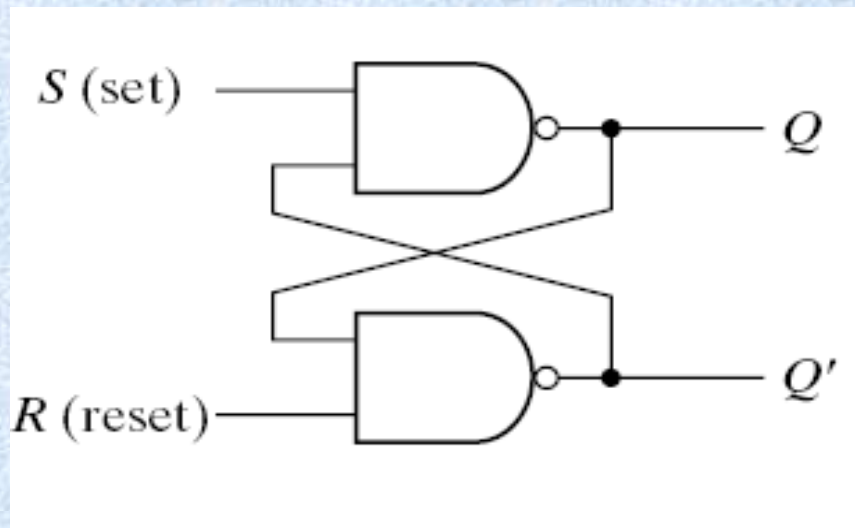


S	R	Q	Q'
1	0	0	1
1	1	0	1 (after SR= 10)
0	1	1	0
1	1	1	0(after SR=01)
0	0	1	1 (Disallowed)

The clocked R-S flip-flop

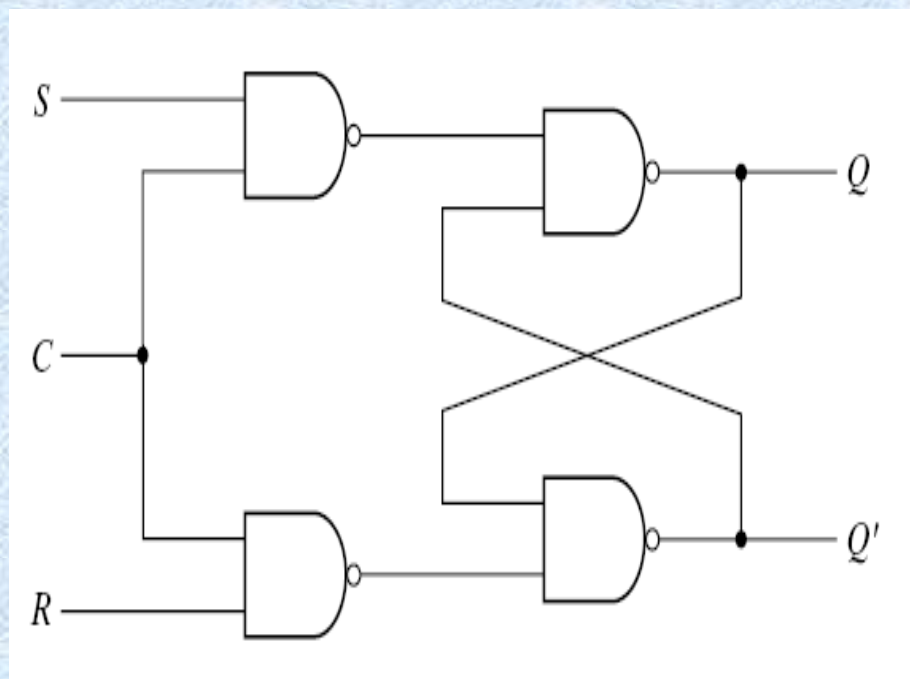


C	S	R	Next state of Q
0	X	X	No change
1	0	0	No change
1	0	1	$Q = 0$; Reset state
1	1	0	$Q = 1$; set state
1	1	1	Indeterminate



D flip-flop

 

D	$Q(t+1)$
0	0
1	1

 



JK flip-flop

 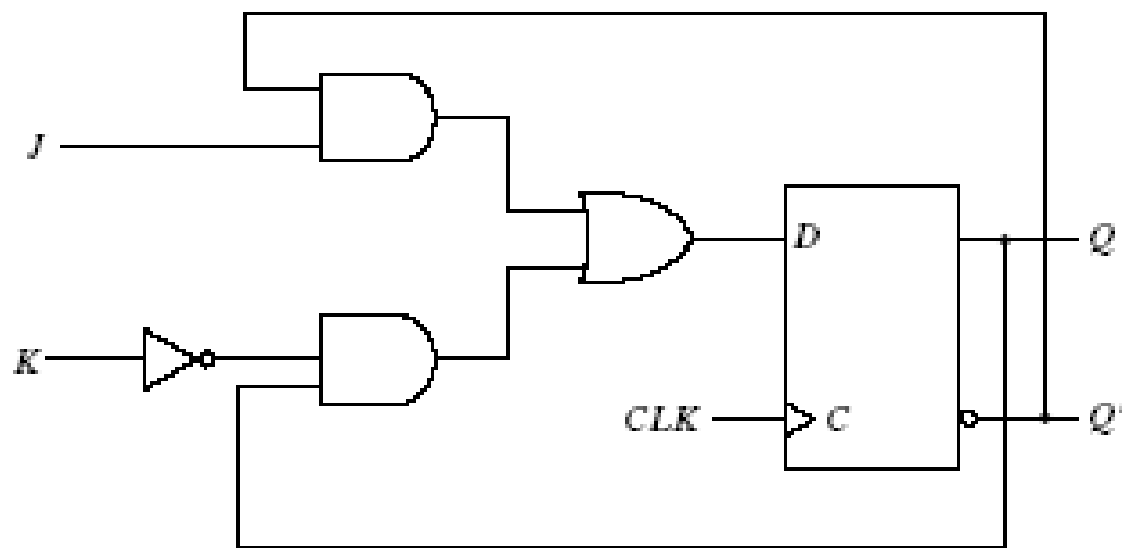


J	K	Q(t+1)
0	0	No change in state
0	1	0
1	0	1
1	1	Complement state

T flip-flop



Q	T	Q(t+1)
0	0	0
0	1	1
1	0	1
1	1	0

  

Flip Flops - with asynchronous inputs

 

Master-Slave Flip-Flop

 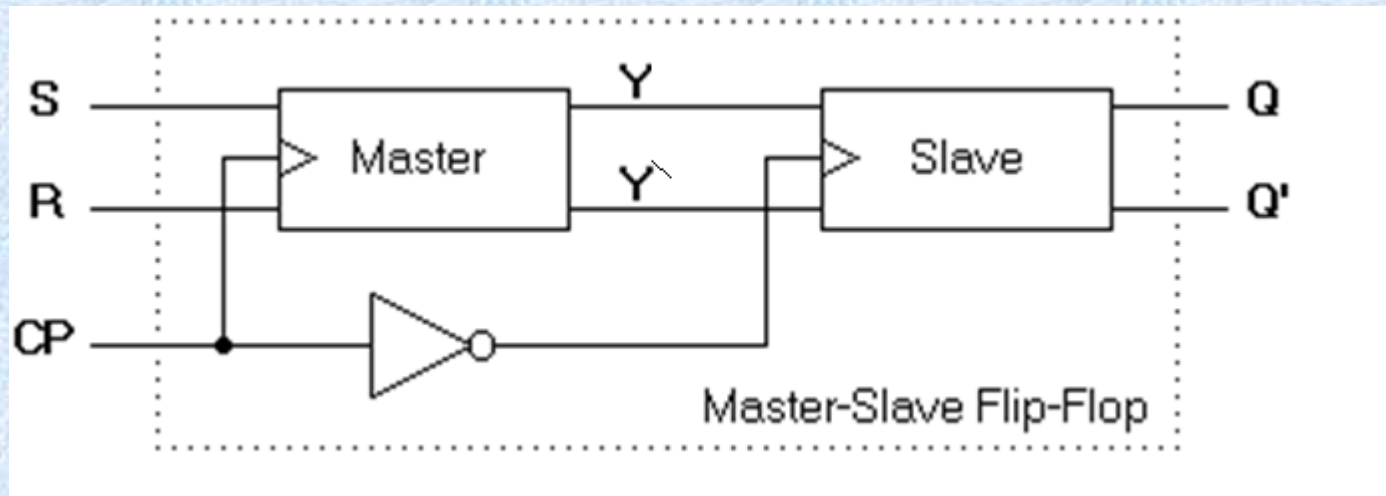

Sequential circuit analysis

- State table
- State diagram
- Timing diagram

What is a “state”?

- The value of the outputs of the flip-flops simultaneously at a given period of time (usually measured after the CP edge arrival).
- Thus if we have two flip-flops, their output will be expressed in two bits (00, 01, 10 and 11)

What is present state and next state?

- Present state is the value of flip-flop output before the arrival of the CP edge.
- Next state is the value of flip-flop output after the arrival of the CP edge.

-

State table

Present State		Next State		Output
Q1(t)	Q2(t)	Q1(t+1)	Q2(t+1)	Y
0	0	0	1	1
0	1	1	0	1
1	0	1	1	0
1	1	0	0	1

Read this state table

Quiz (oral)

Present State		Next State		Output
Q1(t)	Q2(t)	Q1(t+1)	Q2(t+1)	Y(t)
0	0	0	1	1
0	1	1	1	0
1	0	0	0	1
1	1	1	0	0

Read this state table

Present State		Input	Next State		Output
Q1(t)	Q2(t)	X	Q1(t+1)	Q2(t+1)	Y
0	0	0	0	0	1
0	0	1	0	1	1
0	1	0	1	0	0
0	1	1	0	0	1
1	0	0	1	1	0
1	0	1	0	1	1
1	1	0	1	0	0
1	1	1	0	0	1

- 1- Assume we begin at state $Q_1=0$ and $Q_2=0$.
- 2- $X=0$, the next state ($Q_1=0$ and $Q_2=0$) producing $Y=1$.
- 3- $X=1$, the next state ($Q_1=0$ and $Q_2=1$) producing $Y=1$.


Now, can you deduce the next state of the following cases:

- ($Q_1=1$ and $Q_2=0$) and the input $X=0$
- ($Q_1=1$ and $Q_2=0$) and the input $X=1$
- ($Q_1=1$ and $Q_2=1$) and the input $X=0$

Another version of the state table

Present State		Next State <u>X=0</u>		Next State <u>X=1</u>		Output	
Q1(t)	Q2(t)	Q1(t+1)	Q2(t+1)	Q1(t+1)	Q2(t+1)	<u>X=0</u>	<u>X=1</u>
						Y(t)	
0	0	0	0	0	1	1	1
0	1	1	0	0	0	0	1
1	0	1	1	0	1	0	1
1	1	1	0	0	0	0	1



State Diagram

 



Now, can you deduce the next state of the following cases:

- Present state 11 and the input =0
- Present state 11 and the input =1
- Present state 10 and the input =0

State Diagrams of Various Flip-flops

  


State Diagrams of Various Flip-flops

  

Converting from state diagram into state table

Present State		Next State <u>X=0</u>		Next State <u>X=1</u>		Output	
Q1(t)	Q2(t)	Q1(t+1)	Q2(t+1)	Q1(t+1)	Q2(t+1)	<u>X=0</u>	<u>X=1</u>
0	0	0	0	0	1	1	1
0	1	1	0	0	0	0	1
1	0	1	1	0	1	0	1
1	1	1	0	0	0	0	1

 
Converting from state diagram into state table



Sequential Circuit Analysis

- We start with the logic diagram of the circuit which we can derive the input equations for each flip-flop.
- Then, to obtain next-state equations according to the input equations and the type of flip-flop.
- The output variable(s) equations can also be derived from the schematic, and once we have our output and next-state equations, we can generate the next-state and output tables as well as state diagrams.


Example 1:

 


Example 1:

- From the figure, the inputs of the flip flops are:
- $D_1 = X' + Q_1$
- $D_2 = X.Q_2' + X'.Q_1'$
- The output Z equation is:
 - $Z = X * Q_1$

Present State		Input	Next State		Output
Q1(t)	Q2(t)	X	Q1(t+1)	Q2(t+1)	Z
0	0	0	1	1	0
0	0	1			
0	1	0			
0	1	1			
1	0	0			
1	0	1			
1	1	0			
1	1	1			

 

Example 2:

 

- $A(t+1) = DA = A(t).X(t) + B(t).X(t)$

- $B(t+1) = DB = A'(t).X(t)$


- The output Y equation is:

$$Y(t) = X'(t).(B(t) + A(t))$$

Present State		Input	Next State		Output
Q1(t)	Q2(t)	X	Q1(t+1)	Q2(t+1)	Z
0	0	0	0	0	0
0	0	1			
0	1	0			
0	1	1			
1	0	0			
1	0	1			
1	1	0			
1	1	1			

Present State $A(t) \ B(t)$	Next State		Output	
	$x(t)=0$	$x(t)=1$	$x(t)=0$	$x(t)=1$
	$A(t+1)B(t+1)$	$A(t+1)B(t+1)$	$y(t)$	$y(t)$
0 0	0 0	0 1	0	0
0 1	0 0	1 1	1	0
1 0	0 0	1 0	1	0
1 1	0 0	1 0	1	0

Example 3:

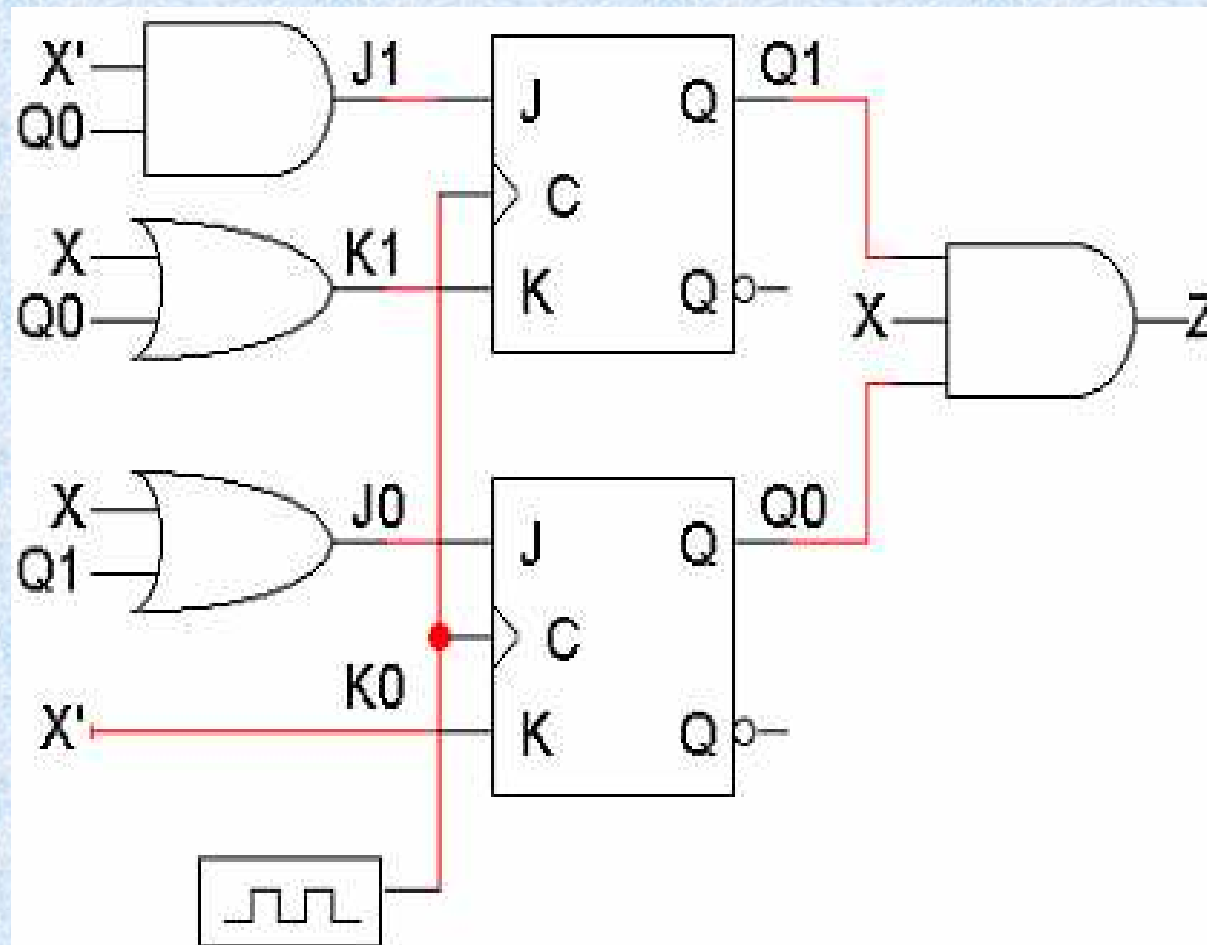

For the first flip flop:

$$J_1 = X'(t) \cdot Q_0(t)$$

$$K_1 = X(t) + Q_0(t)$$

For the second flip flop:

$$J_0 = X(t) + Q_1(t)$$

$$K_0 = X'(t)$$

The output

$$Z = Q_1(t) \cdot X(t)$$

Present State		Inputs X	Flip-flop Inputs			
Q ₁	Q ₀		J ₁	K ₁	J ₀	K ₀
0	0	0	0	0	0	1
0	0	1	0	1	1	0
0	1	0	1	1	0	1
0	1	1	0	1	1	0
1	0	0	0	0	1	1
1	0	1	0	1	1	0
1	1	0	1	1	1	1
1	1	1	0	1	1	0

Build the state table for PS, inputs and flip-flop inputs

Complete the state table for NS, using inputs and flip-flop inputs and excitation table


J	K	Q(t+1)	Operation
0	0	Q(t)	No change
0	1	0	Reset
1	0	1	Set
1	1	Q'(t)	Complement

Present State		Inputs X	FF Inputs				Next State	
Q ₁	Q ₀		J ₁	K ₁	J ₀	K ₀	Q ₁	Q ₀
0	0	0	0	0	0	1	0	0
0	0	1	0	1	1	0	0	1
0	1	0	1	1	0	1	1	0
0	1	1	0	1	1	0	0	1
1	0	0	0	0	1	1	1	1
1	0	1	0	1	1	0	0	1
1	1	0	1	1	1	1	0	0
1	1	1	0	1	1	0	0	1


Complete the state table for output Z, using PS inputs and X input

Present State		Inputs	FF Inputs				Next State		Outputs
Q_1	Q_0	X	J_1	K_1	J_0	K_0	Q_1	Q_0	Z
0	0	0	0	0	0	1	0	0	0
0	0	1	0	1	1	0	0	1	0
0	1	0	1	1	0	1	1	0	0
0	1	1	0	1	1	0	0	1	0
1	0	0	0	0	1	1	1	1	0
1	0	1	0	1	1	0	0	1	0
1	1	0	1	1	1	1	0	0	0
1	1	1	0	1	1	0	0	1	1

Draw the state diagram from state table

 


Report


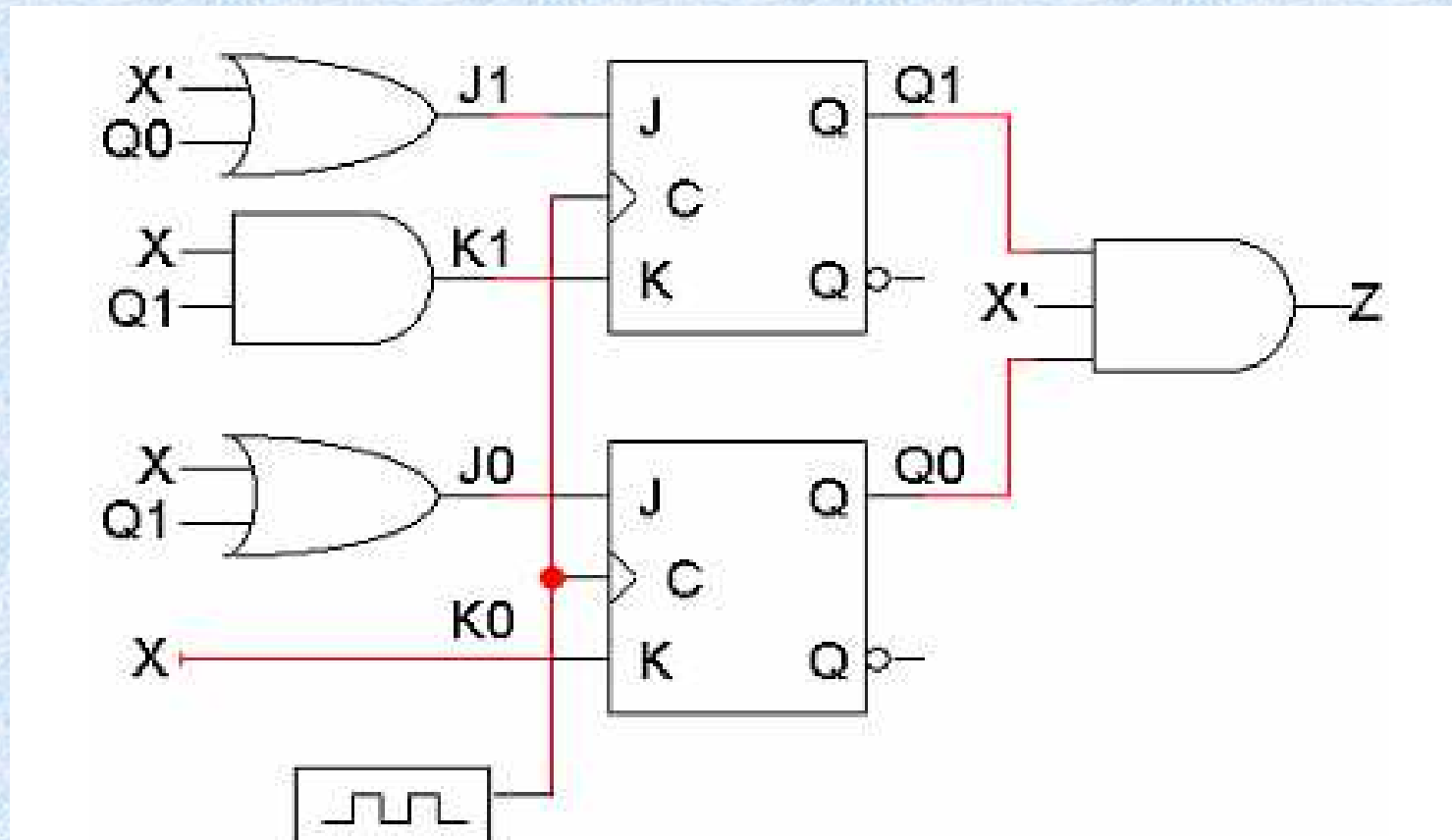


Mealy and Moore state diagrams


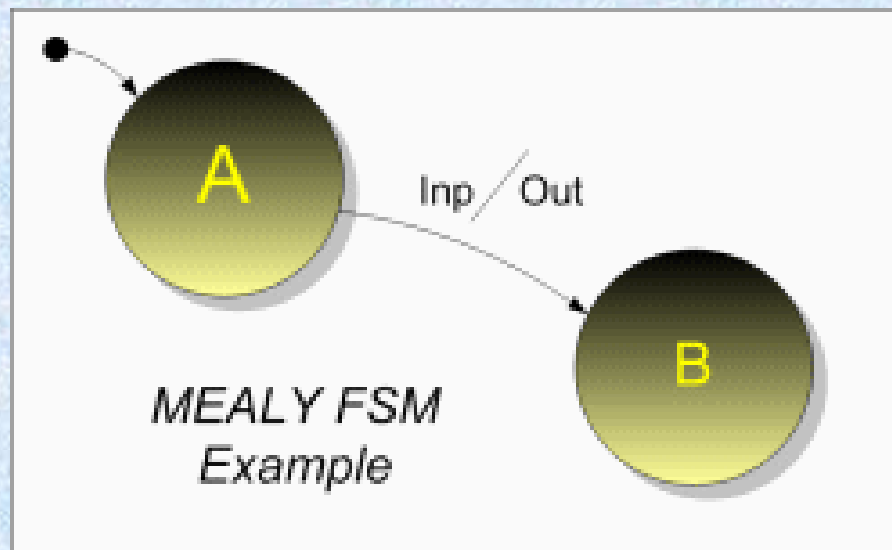
- A **Mealy circuit** (sometimes called **machine**) generates an output based on its current state *and* input. This means that the state diagram will include both input and output signals for each transition edge.




Mealy circuit

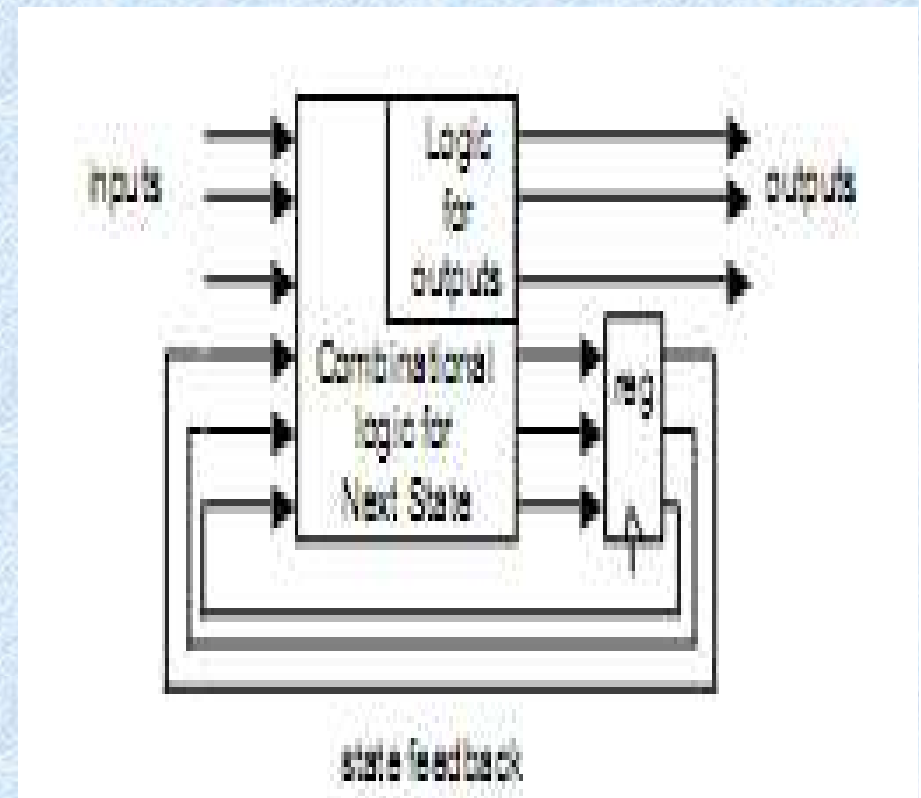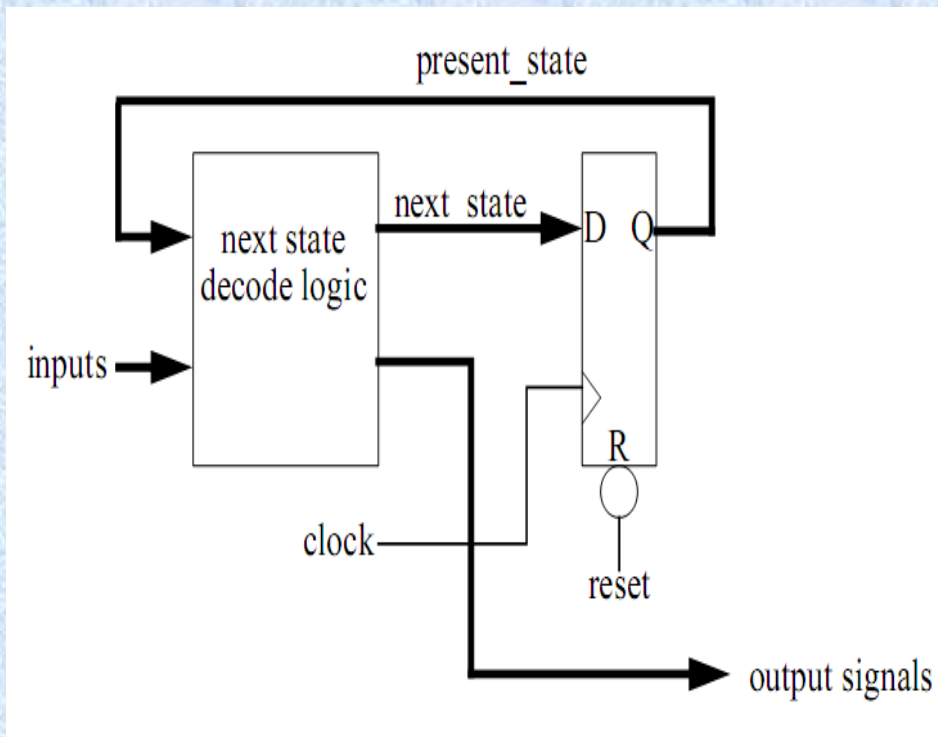


Mealy circuit

  


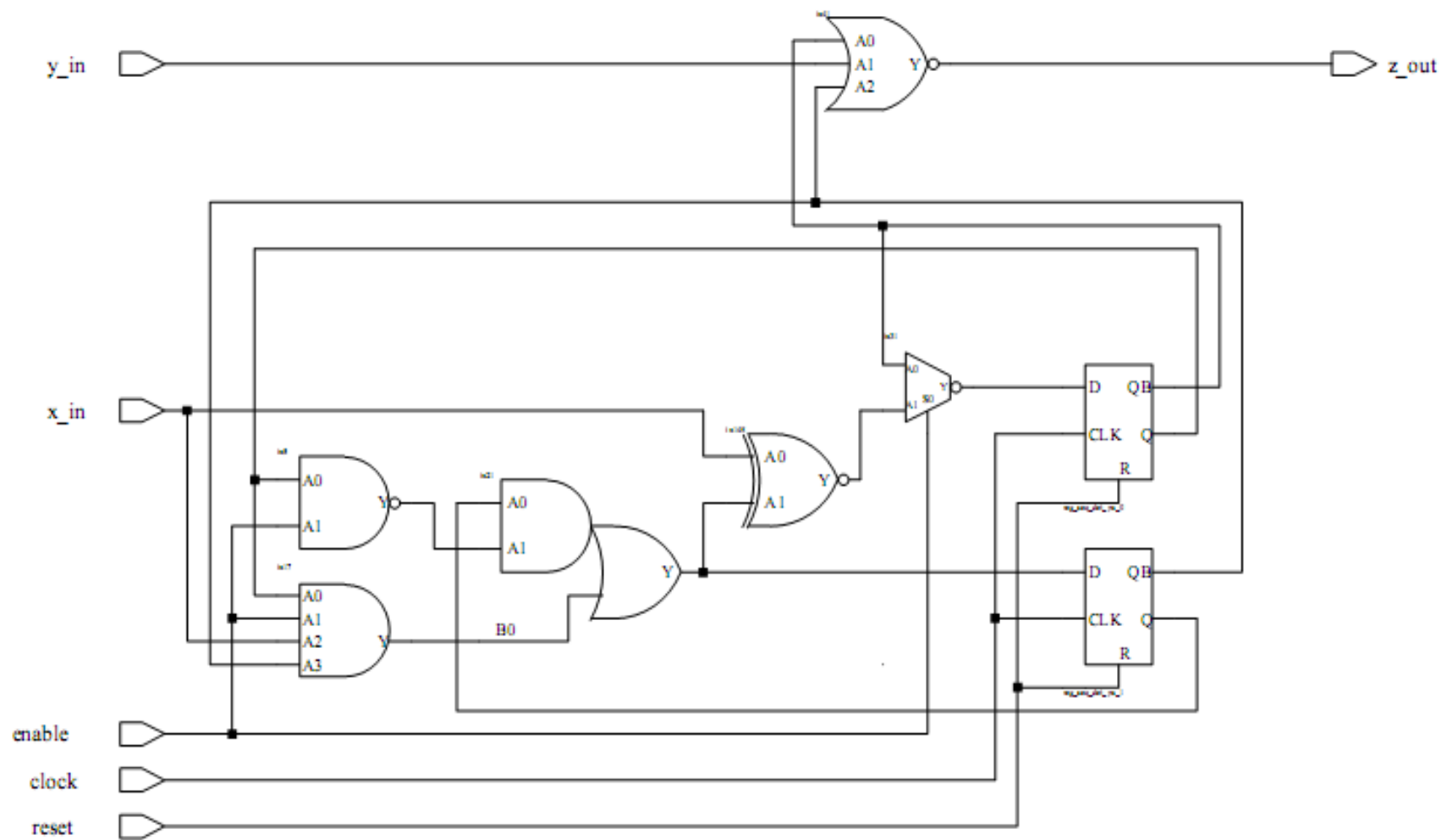


Moore circuit

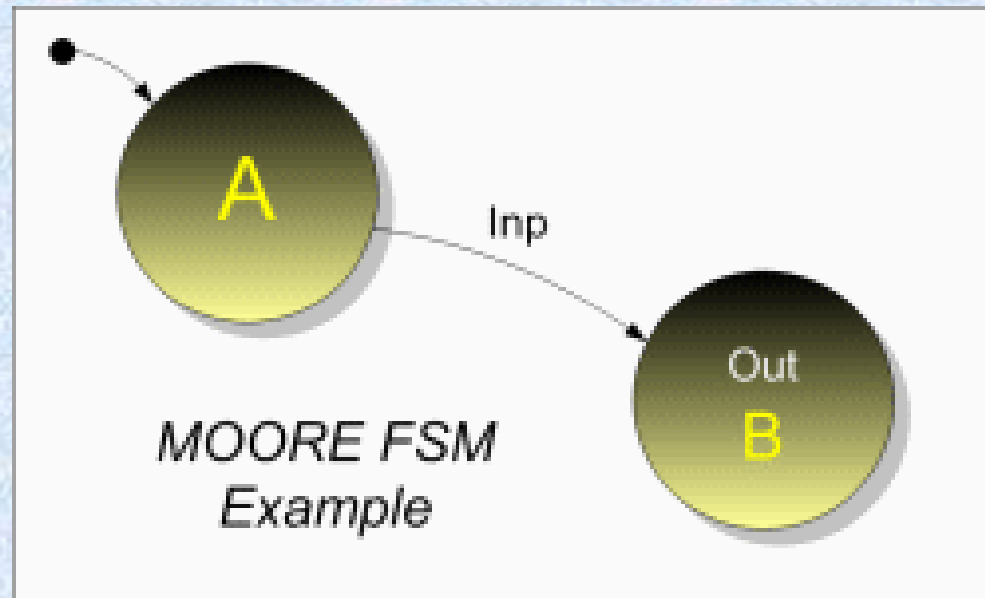
- The output of a Moore finite state machine depends only on the machine's current state; transitions are not directly dependent upon input. The outputs react at the edges of clock pulse.



Moore circuit

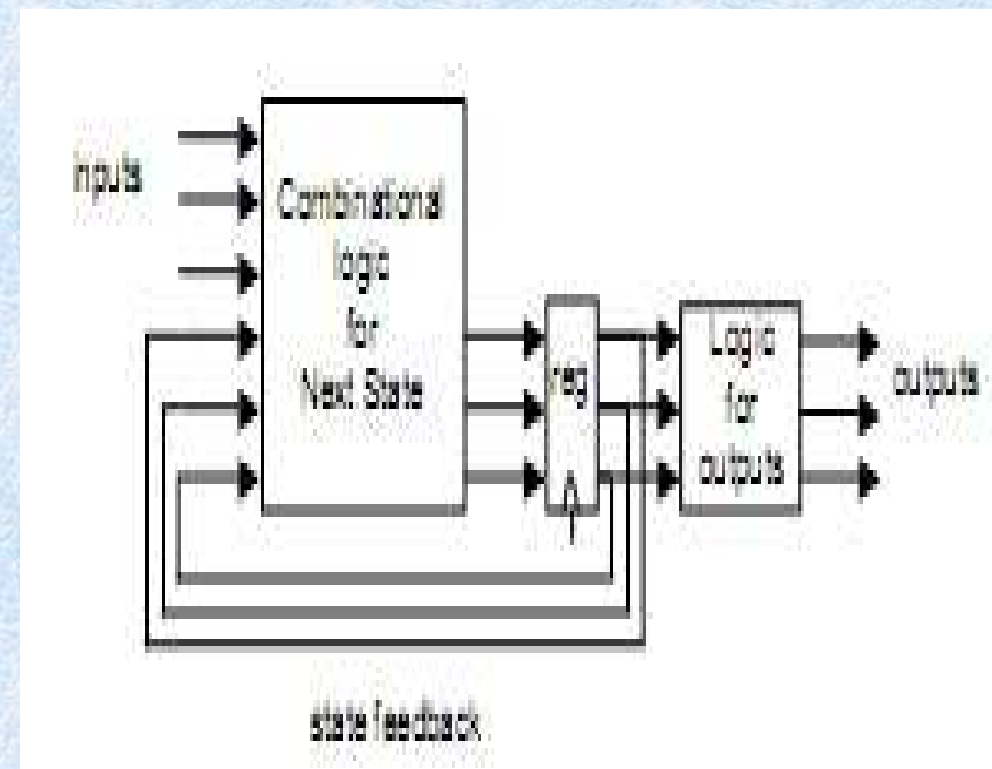 

Moore circuit

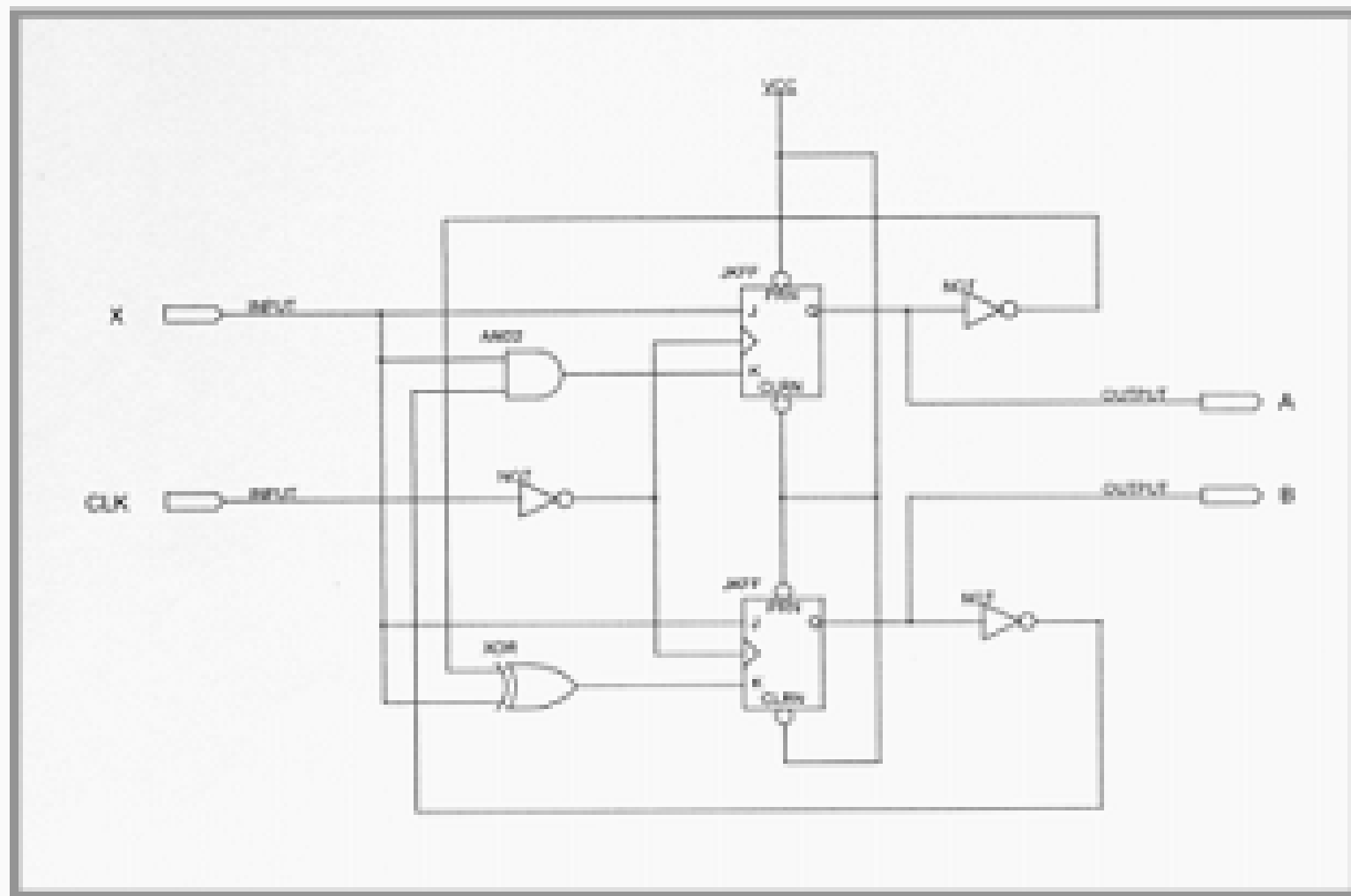

State diagram reduction and assignment

Present State	Next State		Output	
	X=0	X=1	X=0	X=1
S0	S1	S2	0	0
S1	S3	S4	0	0
S2	S5	S6	0	0
S3	S7	S8	0	0
S4	S9	S10	0	0
S5	S11	S12	0	0
S6	S13	S14	0	0
S7	S0	S0	0	0
S8	S0	S0	0	0
S9	S0	S0	0	0
S10	S0	S0	1	0
S11	S0	S0	0	0
S12	S0	S0	1	0
S13	S0	S0	0	0
S14	S0	S0	0	0

Present State	Next State		Output	
	X=0	X=1	X=0	X=1
S0	S1	S2	0	0
S1	S3	S4	0	0
S2	S5	S6	0	0
S3	S7	S8	0	0
S4	S9	SA	0	0
S5	S11	SA	0	0
S6	S13	S14	0	0
S7	S0	S0	0	0
S8	S0	S0	0	0
S9	S0	S0	0	0
S11	S0	S0	0	0
SA	S0	S0	1	0
S13	S0	S0	0	0
S14	S0	S0	0	0


Present State	Next State		Output	
	X=0	X=1	X=0	X=1
S0	S1	S2	0	0
S1	S3	S4	0	0
S2	S5	S6	0	0
S3	SB	SB	0	0
S4	SB	SA	0	0
S5	SB	SA	0	0
S6	SB	SB	0	0
SB	S0	S0	0	0
SA	S0	S0	1	0

Quiz

Present State	Next State		Output	
	X=0	X=1	X=0	X=1
a	c	f	0	0
b	d	e	0	0
c	h	g	0	0
d	b	g	0	0
e	e	b	0	1
f	f	a	0	1
g	c	g	0	1
h	c	f	0	0

Next state and Output sequence for a given input stream

- If we are given a specific sequence of inputs, the state diagram and/or state table, we can predict the sequence of states response to this input sequence and the output sequence too.
- Sequence of $X = \{ 0, 0, 1, 1, 0, 1, 0 \}$. Start state = (01).
- When $X = 0$ at state (01), then the next state is (11), and the output is 0.
- The next value of $X = 0$ and now we are at state (11), then the next state is (10), and the output is 0.
- The next value of $X = 1$ and now we are at state (10), then the next state is (11), and the output is 1.

 

If we have a sequence of $X = \{ 0, 1, 1, 0, 0, 1, 1 \}$.
Start state = (b).

Present State	Next State		Output	
	X=0	X=1	X=0	X=1
a	c	f	0	0
b	d	e	0	0
c	a	g	0	0
d	b	g	0	0
e	e	b	0	1
f	f	a	0	1
g	c	g	0	1